

1. Half Adder

A Half Adder is a combinational circuit that performs binary addition of two bits. It produces two outputs: a sum (S) and a carry (C).

Logic Equations:

- Sum (S) = A XOR B
- Carry (C) = A * B

Truth Table:

A B Sum Carry

0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Applications:

- Basic binary addition circuits
- Building blocks for full adders

Diagram: XOR gate for Sum, AND gate for Carry

2. Full Adder

A Full Adder adds three binary bits: A, B, and Carry-in (Cin). It produces two outputs: a sum (S) and a carry-out (Cout).

Logic Equations:

- Sum = A XOR B XOR Cin
- Carry = AB + BCin + ACin

Truth Table:

A B Cin Sum Carry

0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Applications:

- Used in arithmetic logic units for multi-bit addition

Diagram: Two XORs, two ANDs, one OR gate

3. Half Subtractor

A Half Subtractor subtracts binary digit B from A. It produces two outputs: Difference (D) and Borrow (B).

Logic Equations:

- Difference = A XOR B
- Borrow = NOT A AND B

Truth Table:

A B Diff Borrow

0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

Applications:

- Simple binary subtraction logic

Diagram: XOR gate for difference, NOT + AND for borrow

4. Full Subtractor

A Full Subtractor performs subtraction of A - B - Bin (borrow-in). It has three inputs and produces a Difference and Borrow output.

Logic Equations:

- Difference = A XOR B XOR Bin
- Borrow = NOT A * B + Bin * NOT (A XOR B)

Truth Table:

A B Bin Diff Borrow

0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Applications:

- Binary subtraction with borrow management

Diagram: Logic blocks with XOR, NOT, AND, OR gates

5. Multiplexer (MUX)

A Multiplexer selects one input from multiple and sends it to the output, based on select lines.

Example: 4-to-1 MUX

Inputs: I0, I1, I2, I3

Select Lines: S1, S0

Output Equation:

$$Y = I0 \cdot S1' \cdot S0' + I1 \cdot S1' \cdot S0 + I2 \cdot S1 \cdot S0' + I3 \cdot S1 \cdot S0$$

Truth Table:

S1 S0 Y

0	0	I0
0	1	I1
1	0	I2
1	1	I3

Applications:

- Data routing
- CPU control logic

Diagram: MUX block with data lines and selectors

6. Demultiplexer (DEMUX)

A Demultiplexer takes one input and distributes it to one of several outputs.

Example: 1-to-4 DEMUX

Input: D

Select Lines: S1, S0

Outputs:

- $Y0 = D \cdot S1' \cdot S0'$
- $Y1 = D \cdot S1' \cdot S0$
- $Y2 = D \cdot S1 \cdot S0'$
- $Y3 = D \cdot S1 \cdot S0$

Applications:

- Memory writing control
- Data line switching

Diagram: DEMUX block with one input and multiple outputs

7. Encoder

An Encoder converts multiple input lines into a smaller number of output lines (binary code).

Example: 4-to-2 Encoder

D3 D2 D1 D0 A1 A0

1	0	0	0	1	1
0	1	0	0	1	0
0	0	1	0	0	1
0	0	0	1	0	0

Applications:

- Keyboard scanners
- Data compression

Diagram: Block diagram with 4 inputs and 2 outputs

8. Decoder

A Decoder performs the reverse of an encoder. It converts n binary inputs into 2^n outputs.

Example: 2-to-4 Decoder

A B Y0 Y1 Y2 Y3

0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

Applications:

- Memory address decoding
- Instruction decoding

Diagram: Block with 2 inputs and 4 outputs